

Quad linear  
FAN-IN-FAN OUT

Digitizer

Tagger

CH1

CFTD

Delayed

CH0

Scatterer

CH2

CFTD

Delayed

LOGIC  
UNIT

TRG IN

Detector

CH3

CFTD

Delayed

CH1

CH2

